

Creating Schmitt-Triggered Inputs on the Propeller P8X32A Microcontroller

Abstract: Schmitt-triggering diminishes or eliminates logic-level uncertainty from signals having slow rise/fall times and those burdened with superimposed noise. It achieves this using positive feedback to create a hysteresis band about the threshold of a logic input, which must be crossed in its entirety to effect a state change. With the addition of external resistors, along with programmed positive feedback, the P8X32A can enjoy the benefits of Schmitt-triggering on any of its inputs.

Introduction


The Propeller P8X32A's digital input logic thresholds are fixed at approximately $V_{DD}/2$, without any hysteresis and without a way to configure them for Schmitt triggering. With the addition of a couple external resistors per input and by committing one separate pin for feedback, any number of Propeller inputs can gain Schmitt-triggering capability.

Schmitt Trigger Principle

The inputs of a Schmitt-triggered logic device exhibit hysteresis. This is to say that if a rising voltage on an input first registers as a logic "1" at some threshold V_{HI} , and if a falling voltage on the input first registers as a logic "0" at some threshold V_{LO} , the input displays hysteresis if $V_{HI} > V_{LO}$. The area between the two thresholds is known as the "hysteresis band."


Hysteresis is a valuable digital input characteristic when presented with signals having slow rise or fall times or with signals carrying superimposed noise voltages. Without hysteresis, small variations in the input voltage near a gate's logic threshold, V_{TH} , can cause multiple logic transitions on its output. Adding hysteresis can reduce or eliminate this problem, as Figure 1 illustrates.

Figure 1: Hysteresis Band with Schmitt-triggered Input

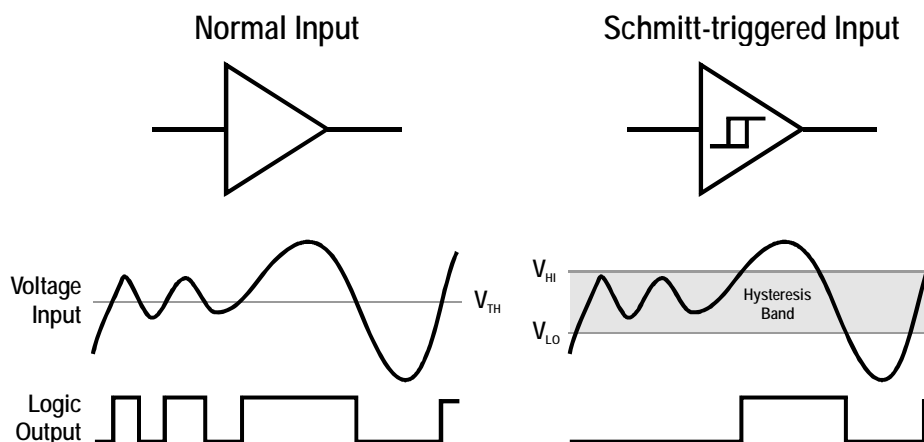

The equivalent circuit for a Schmitt trigger consists of a normal logic buffer with a resistor in its input path and another resistor feeding back from its output, as shown in Figure 2.

Figure 2: Equivalent circuit for a Schmitt Trigger

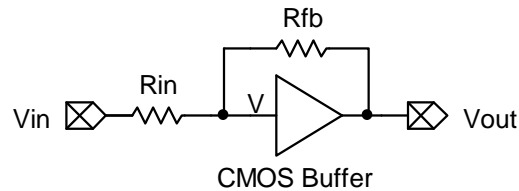

In this schematic, the voltage V at the buffer's input satisfies the following equation:

$$\frac{V_{out} - V}{R_{fb}} = \frac{V - V_{in}}{R_{in}} \quad \text{Equation 1}$$

To compute the V_{HI} and V_{LO} thresholds, solve Equation 1 for V_{in} , substitute the buffer's threshold voltage, V_{TH} , for V , then compute for $V_{out} = 0$ and $V_{out} = V_{dd}$, respectively:

$$V_{in} = \frac{(R_{in} + R_{fb})V_{TH} - R_{in}V_{out}}{R_{fb}} \quad \text{Equation 2}$$

$$V_{HI} = \frac{(R_{in} + R_{fb})V_{TH}}{R_{fb}} \quad \text{Equation 3: output low}$$


$$V_{LO} = \frac{(R_{in} + R_{fb})V_{TH} - R_{in}V_{dd}}{R_{fb}} \quad \text{Equation 4: output high}$$

For example, for $V_{dd} = 3.3 \text{ V}$, $V_{TH} = 1.5 \text{ V}$, $R_{in} = 510 \text{ } \Omega$, and $R_{fb} = 5.1 \text{ k}\Omega$, the hysteresis band would extend from $V_{LO} = 1.32 \text{ V}$ to $V_{HI} = 1.65 \text{ V}$. Also note from the above equations that the width of the hysteresis band, $V_{HI} - V_{LO} = R_{in}V_{dd} / R_{fb}$, depends only upon the ratio of the two resistor values and the value of V_{dd} .

Propeller Hardware Implementation

Figure 3 shows the Propeller equivalent of Figure 2.

Figure 3: Propeller Schmitt Trigger Circuit

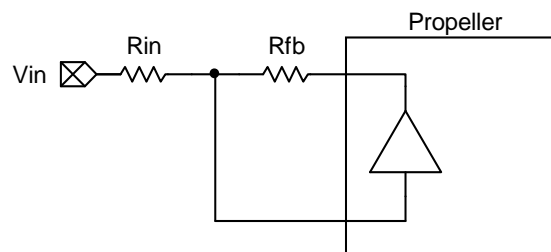


In this schematic, two Propeller pins provide the Schmitt-triggering function: one for the input; the other for the feedback output. The internal “buffer” does not exist as an actual circuit but, rather, as a software function. Moreover, this buffering does not even need to be continuous but can take place only when it’s necessary to read the input pin. It works like this:

1. Apply the input previously read from the input pin to the feedback pin.
2. Read the input pin.
3. Save the reading from step 2 for the next iteration of step 1.

The input (high or low) read in step 2 will effectively be Schmitt-triggered.

Because the feedback does not have to be continuous, a single feedback pin can operate in conjunction with any number of input pins, as long as those pins do not need to be read simultaneously, as Figure 4 illustrates.

Figure 4: Multiple Inputs with a Single Feedback Pin

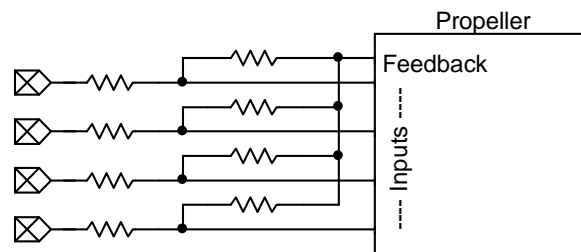

Applying the previous reading for each input pin, in succession, to the feedback pin and then reading that input pin results in a reading of the pins’ Schmitt-triggered states.

Propeller Software Implementation

The Spin implementation of Schmitt triggering is quite simple, consisting of two lines:

```
outa[FB_PIN] := pin_state
pin_state := ina[INP_PIN]
```

In this code snippet, **pin_state** is a variable that keeps track of the latest state (0 or 1) read from the pin denoted by **INP_PIN**. The pin number of the feedback pin is **FB_PIN**.

In Propeller Assembly language (PASM), it is import not to read the input state too soon after setting the feedback pin. This is due to the low-pass filter created by the feedback resistor and the Propeller pin’s input capacitance. The next example illustrates Schmitt triggering in PASM.

```
'Initial setup:
        or          dira,fb_mask          'Make the feedback pin an output.
'Pin reading:
        test       pin_state,#1 wc       'Set carry from pin_state bit 0.
        muxc      outa,fb_mask           'Copy carry to feedback pin.
        nop                                     'Wait for things to settle...
```

```
        nop
        nop
        mov     pin_state,ina      'Read the pins.
        shr     pin_state,#INP_PIN 'Shift input pin's state to bit 0.

'Variables:

fb_mask    long     1 << FB_PIN   'Bit mask for feedback pin.
pin_state  long     0              'Current value of pin.
```

In the example above, `pin_state`, `INP_PIN`, and `FB_PIN` have the same meanings as before.

Resources

Download the example Spin code zip archive: www.parallaxsemiconductor.com/an015.

Revision History

Version 1.0: original document.

Parallax, Inc., dba Parallax Semiconductor, makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does Parallax, Inc., dba Parallax Semiconductor, assume any liability arising out of the application or use of any product, and specifically disclaims any and all liability, including without limitation consequential or incidental damages even if Parallax, Inc., dba Parallax Semiconductor, has been advised of the possibility of such damages. Reproduction of this document in whole or in part is prohibited without the prior written consent of Parallax, Inc., dba Parallax Semiconductor.

Copyright © 2011 Parallax, Inc. dba Parallax Semiconductor. All rights are reserved.
Propeller and Parallax Semiconductor are trademarks of Parallax, Inc.